

Course Number	ELE404
Course Title	Electronic Circuits I
Semester/Year	W2024
Instructor	Fei Yuan
Section Number	15

## Design Project

Report Title	Amplifier Design Project
Group Number	
Submission Date	2024-04-07
Due Date	2024-04-07

Student Name	Student ID (xxxx1234)
Jason Su	501158090

## **Table of Content**

<b>1. Introduction.....</b>	<b>3</b>
<b>2. Objectives.....</b>	<b>3</b>
<b>3. Circuit under Test.....</b>	<b>3</b>
<b>4. Experimental Results.....</b>	<b>6</b>
<b>5. Conclusions and Remarks.....</b>	<b>9</b>
<b>6. Appendix: Manual Calculations.....</b>	<b>10</b>

## 1. Introduction

The final report for the design project, Amplifier Design Project, is presented herein. The lab took place on March 27th, 2024 and is due on April 7th, 2024. This lab tests all course material regarding Bipolar-Junction Transistors (BJT), and requires the implementation of a multistage amplifier. The circuit was simulated using Multisim and all calculations can be found in the appendix below (Pg 10).

## 2. Objectives

The objective of this lab was to design, simulate, analyze, implement, and test a single-supply, multistage, inverting, transistor amplifier which fulfills a set of specifications. Bipolar-Junction Transistors in active mode are utilized to create the multistage amplifier. Results were checked with values obtained from the simulated circuit and the specifications requirements below:

- Power supply: **+10V** relative to the ground;
- Quiescent current drawn from the power supply: no larger than **10 mA**;
- No-load voltage gain (at 1 kHz):  $|A_{vo}| = 50 (\pm 10\%)$ ;
- Maximum no-load output voltage swing (at 1 kHz): no smaller than 8 V peak to peak;
- Loaded voltage gain (at 1 kHz and with  $R_L = 1\text{ k}\Omega$ ): no smaller than **90%** of the no-load voltage gain;
- Maximum loaded output voltage swing (at 1 kHz and  $R_L = 1\text{ k}\Omega$ ): no smaller than 4 V peak to peak;
- Input resistance (at 1 kHz): no smaller than **20 k $\Omega$** ;
- Amplifier type: inverting or non-inverting;
- Frequency response: 20 Hz to 50 kHz (**-3dB** response);
- Type of transistors: BJT;
- Number of transistors (stages): no more than 3;
- Resistances permitted: values smaller than **220 k $\Omega$**  from the E24 series;
- Capacitors permitted: **0.1  $\mu\text{F}$ , 1.0  $\mu\text{F}$ , 2.2  $\mu\text{F}$ , 4.7  $\mu\text{F}$ , 10  $\mu\text{F}$ , 47  $\mu\text{F}$ , 100  $\mu\text{F}$ , 220  $\mu\text{F}$** ;
- Other components (BJTs, diodes, Zener diodes, etc.): only from your ELE404 lab kit.

### **Notes:**

- The output voltage must be free from distortions (clipping, etc.) in all test conditions.
- The source resistance,  $R_s$ , must be 600  $\Omega$  for all tests.

## 3. Circuit under Test

**Figure 1** below is a schematic diagram of the test circuit. Thus the amplifier circuit consists of three stages, two Common-Emitter amplifiers back to back and an Emitter-Follower. The two CE amplifiers were chosen to achieve the no load gain of 50 since using a singular CE amplifier would cause too much distortion. The total gain was split between the two CE amplifiers to supply around 7.1 each. This was found from the square root of 50 as the total gain is the product of the gain from each stage, and since voltage gain from a CC (stage 3) is approximately 1. Therefore total gain would be  $7.1 \times 7.1 \times 1 \approx 50$ .

The signal source consists of a signal voltage  $V_s$  with a peak-to-peak voltage of 100 mV (50 mV<sub>pk</sub>) and frequency of 1 kHz, as well as a signal resistor  $R_s$  of 600  $\Omega$ .  $V_1$  represents the  $V_{cc}$  DC voltage of 10 V.

Emitter and collector resistors were chosen first by calculating the current and input resistance of each stage. Emitter resistor  $R_{E5}$  was chosen to be a smaller value so it doesn't

significantly affect the loading properties of the load stage. The emitter degeneration resistors for the first two stages were chosen next by comparing it to the 7.1 gain needed. Finally the six biasing resistors in the voltage dividers were chosen. The resistance was chosen to be large enough to supply negative feedback while still allowing enough current to pass through. A low resistance would cause the input resistance to decrease as well, creating a large loading impact between each stage.

Each stage utilizes a *2N3904 BJT* ( $Q_1, Q_2, Q_3$ ), biasing resistors for the voltage divider, and collector and emitter resistors. Electrolytic capacitors  $C_1, C_3$ , and  $C_5$  are used to bypass AC signals from flowing backwards and have a capacitance of  $10 \mu F$ . These coupling capacitors are used in between stages since input resistances are large. The overall gain of the amplifier could be affected by small changes in the emitter degeneration resistor which is why capacitors  $C_2, C_4$ , and  $C_6$  are instead  $100 \mu F$ , as a higher capacitance is needed for emitter degeneration. The values for the resistors and capacitors are listed in **Tables 1, 2, 3** below:

$R_1 [k\Omega]$	$R_2 [k\Omega]$	$R_3 [k\Omega]$	$R_4 [k\Omega]$	$R_5 [k\Omega]$	$R_6 [k\Omega]$
91	68	91	68	91	200

**Table 1:** Biasing Resistor Values

$R_{C1} [k\Omega]$	$R_{C2} [k\Omega]$	$R_{E1} [k\Omega]$	$R_{E2} [k\Omega]$	$R_{E3} [k\Omega]$	$R_{E4} [k\Omega]$	$R_{E5} [k\Omega]$	$R_L [k\Omega]$
15	13	15	1.5	15	1.3	1	1

**Table 2:** Collector and Emitter Resistor Values


$C_1 [\mu F]$	$C_2 [\mu F]$	$C_3 [\mu F]$	$C_4 [\mu F]$	$C_5 [\mu F]$	$C_6 [\mu F]$
10	100	10	100	10	100

**Table 3:** Capacitor Values



#### 4. Experimental Results


The circuit in **Figure 1** was constructed and simulated in Multisim. The  $V_i$  and  $V_o$  waveforms were then captured with the parameters of the no-load gain  $A_{vo}$  and loaded gain  $A_v$  measured and calculated. Quiescent current drawn from  $V_{cc}$ , the frequency response, and the input resistance were then found and compared to specifications list. **Graph 1, 2, 3, Table 4, 5, 6,** and **Figure 2** and **3** report the results.

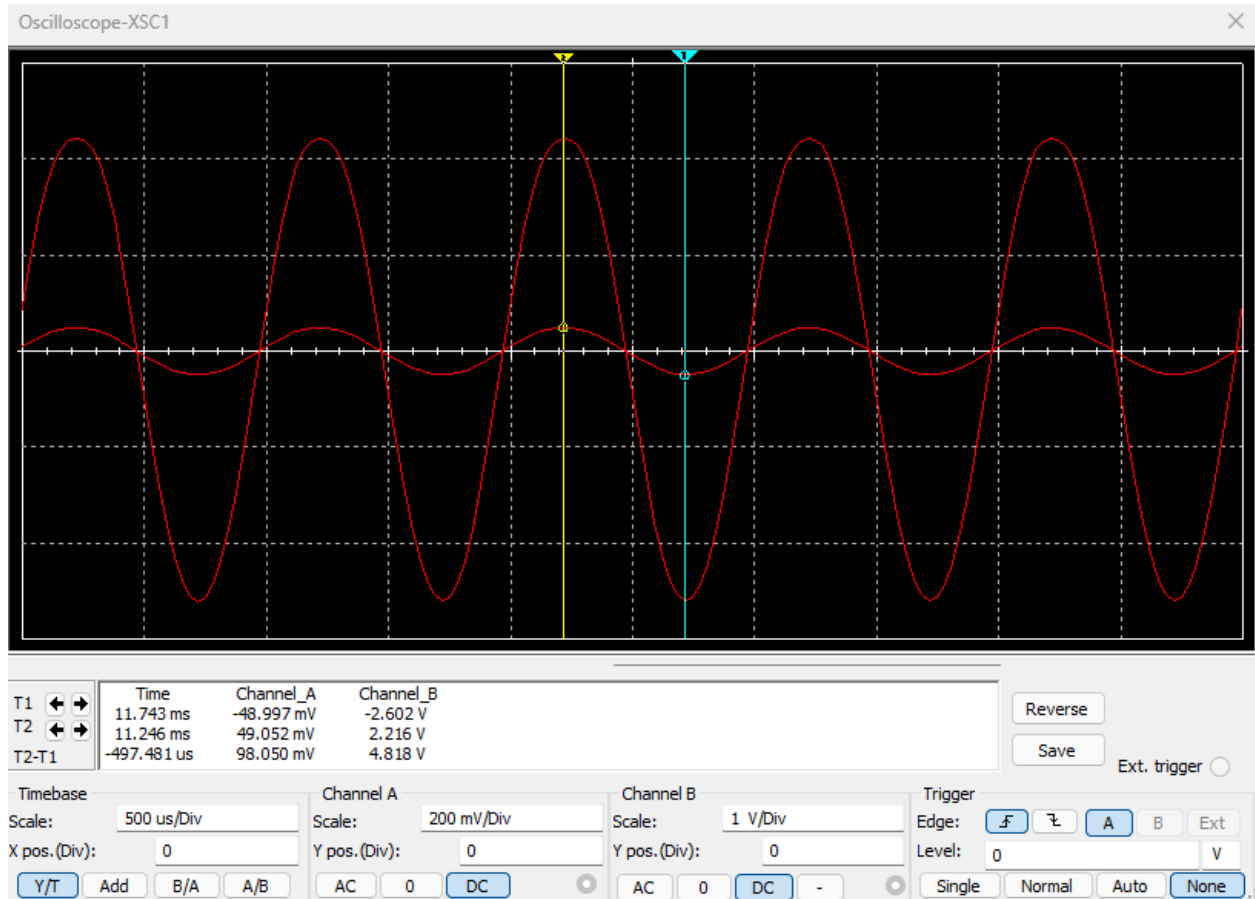

**Graph 1:** Simulated results of  $V_i$  and  $V_o$  for **Figure 1** with no-load ( $R_L = \infty$ ).

$V_{i,pp}$ [V]	$V_{o,pp}$ [V]	$A_{vo}$ [V/V]
0.098	4.818	49.163


**Table 4:** Simulated results of no-load voltage swing for **Figure 1** ( $R_L = \infty$ ).

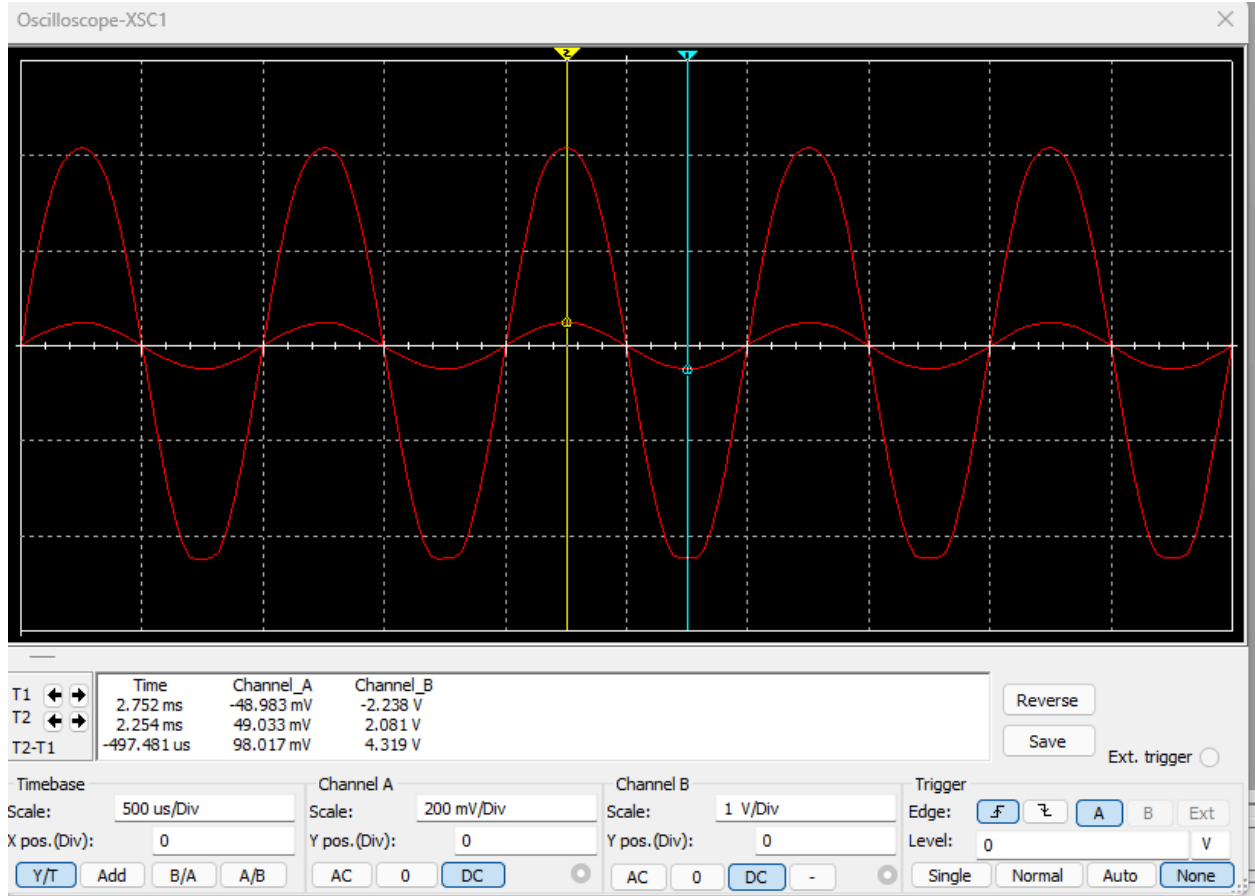


**Graph 2:** Simulated results of  $V_i$  and  $V_o$  for **Figure 1** with load ( $R_L = 1\text{ k}\Omega$ ).

$V_{i,pp}$ [V]	$V_{o,pp}$ [V]	$A_v$ [V/V]
0.098	4.319	44.071

**Table 5:** Simulated results of **loaded** voltage swing for **Figure 1** ( $R_L = 1\text{ k}\Omega$ ).

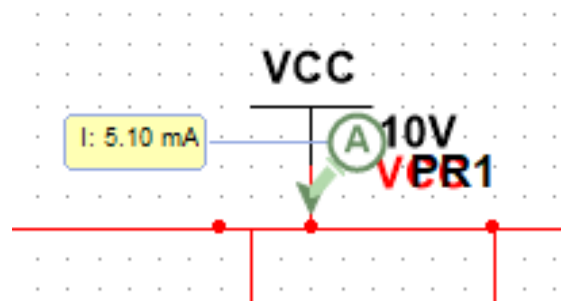

**Figure 2:** Quiescent current drawn from  $V_{cc}$  in **Figure 1** ( $I \leq 10\text{ mA}$ ).

 

Graph 3: Frequency response graph of Figure 1.

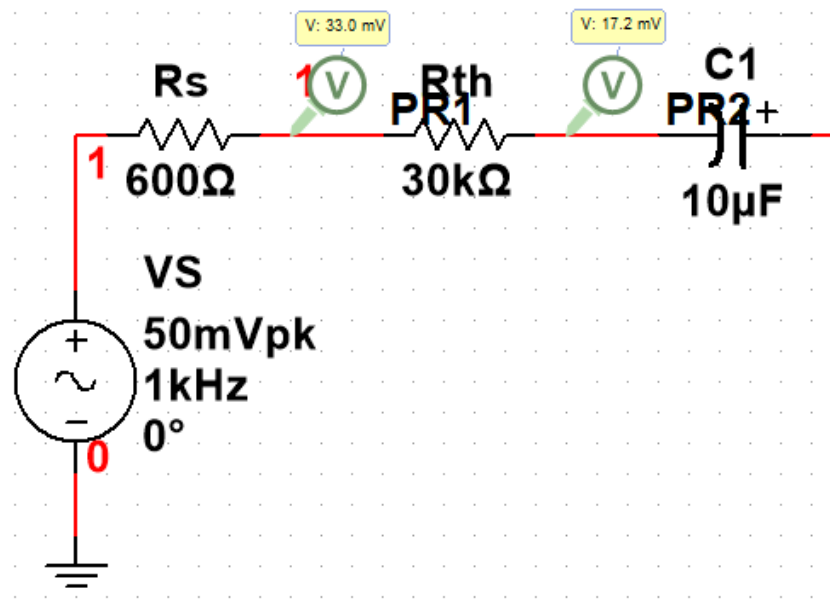


Figure 3: Voltage values of  $V_i$  and  $V_{th}$ .

$R_{th}$ [kΩ]	$V_{th}$ [mVrms]	$V_i$ [mVrms]	$R_{in,measured}$ [kΩ]	$R_{in,calculated}$ [kΩ]
30	33	17.2	32.658	31.195

Table 6: Values from Figure 3 used to measure  $R_{in}$ .



## 5. Conclusions and Remarks

Specification	Calculated Value	Tested Value	% Error	Achieved?
Quiescent current drawn from the power supply: no larger than <b>10 mA</b> ;	5.23 mA	5.10 mA	2.549%	Yes
No-load voltage gain (at 1 kHz): $ A_{vo}  = 50 (\pm 10\%)$ ;	50.41	49.163	2.5365%	Yes
Maximum no-load output voltage swing (at 1 kHz): no smaller than 8 V peak to peak;	8 V	4.818 V <sub>pp</sub>	66.044%	No
Loaded voltage gain (at 1 kHz and with $RL = 1\text{ k}\Omega$ ): no smaller than <b>90%</b> of the no-load voltage gain;	47.57	44.071	7.9395%	Yes
Maximum loaded output voltage swing (at 1 kHz and $RL = 1\text{ k}\Omega$ ): no smaller than 4 V peak to peak;	4 V	4.319 V <sub>pp</sub>	7.386%	Yes
Input resistance (at 1 kHz): no smaller than <b>20 k<math>\Omega</math></b> ;	31.195 k $\Omega$	32.658 k $\Omega$	4.4798%	Yes
Frequency response: 20 Hz to 50 kHz ( <b>-3dB</b> response);	–	<b>Graph 3</b>	–	Yes

When comparing values measured from **Figure 1** to values manually calculated, it is seen that the majority of the specifications have been met with a relatively small percent error. The maximum no-load output voltage swing is the only specification not met as the tested value is not greater than 8 V peak to peak. This could be due to error in calculations or in the simulation where the biasing of each stage may differ. Another likely case is that the operating point chosen is too close to the threshold voltage as the output voltage is not able to swing a full 8 volts. This could also be resolved if a lower frequency was used as  $V_S$  as it would allow the output voltage to swing more. The other percent errors could be due to calculation errors such as rounded resistance values to meet the E24 series requirement. Besides the one discrepancy, all other specifications were met with a percent error less than 10%, meaning that the circuit and calculations used were proven effective and successful.

## 6. Appendix - Calculations

No load Voltage gain:  $|A_{vo}| = 50 \pm 10\%$

Max No load output Voltage Swing:  $V_{pp} \geq 8V$

Loaded Voltage gain ( $R_L = 1k\Omega$ ):  $A_v \geq 90\%$  of  $A_{vo}$

Max loaded output voltage swing ( $R_L = 1k\Omega$ ):  $V_{pp} \geq 4V$

input resistance:  $R_{in} \geq 20k\Omega$

Must be CE to CE to CC

### Gain Distribution

$V_{CC} = 10V$   
 $I_{DC} \leq 10mA$   
 $A_{vo} = 50 \pm 5 (10\%)$   
 $V_o \geq 8V_{pp}$   
 $V_c \geq 4V_{pp}$   
 $R_{in} \geq 20k\Omega$   
 all  $R \leq 220k\Omega$

$A_{vtotal} = A_{v1} \cdot A_{v2} \cdot A_{v3}$   
 Voltage Gain of CC  $\approx 1 \therefore A_{v3} \approx 1$

$50 = A_{v1} \cdot A_{v2} \cdot 1$

$\sqrt{50} \approx 7.1$

$A_{v1} = A_{v2} = 7.1$

$\hookrightarrow A_{v1} = \frac{V_2}{V_1} = -7.1$

$A_{v2} = \frac{V_4}{V_3} = -7.1$

} negative since CE is inverting.

$-ve \times -ve \times +ve = +ve$

$\therefore$  Final output is Non-inverting

### Stage 1 & 2 (CE)

$A_{v1} = A_{v2}$

$\therefore I_{C1} \text{ \& } I_{C2} = 400\mu A$  from load line.

$g_m = \frac{I_C}{V_T} = \frac{400\mu A}{26mV} = 0.01545$

$I_B = 3.5\mu A$

$\beta = \frac{400\mu A}{3.5\mu A} = 114.3$

$I_{B,DC} = 2\mu A$  (for quiescent)

### Stage 3 (CC)

Assuming  $R_{ES} = 1k\Omega$  (same as  $R_L$ )

$g_m = \frac{10mA}{26mV} = 0.385$

$I_C = 10mA$  } from load line

$I_B = 65\mu A$  }

$\beta = \frac{I_C}{I_B} = \frac{10mA}{65\mu A} = 153.8$

Using  $91k\Omega$  for  $R_S$


• From E24 Series

•  $V_B$  shouldn't be affected

• Divider current  $\gg I_B$

$I_{B,DC} = 30\mu A$  (quiescent)

### KCL @ $V_s$

 


$$\frac{5-10}{91k} + \frac{5}{R_G} + 30\mu A = 0$$

$$-24.945\mu A + \frac{5}{R_G} = 0$$

$$R_G = \frac{5V}{24.945\mu A}$$

$$R_G = 200k\Omega$$

### Stage 2 kVL

 

$$-4.25 + 0.7 + I_E \cdot R_{E3} = 0$$

$$-3.55 + (1 + 114.3) 2\mu A R_{E3} = 0$$

$$R_{E3} \approx 15k\Omega$$

$$I_{C,DC} = \frac{V_{CC}}{R_C + R_{E3}}$$

$$R_C + R_{E3} = \frac{10V}{400\mu A} = 25k\Omega$$

$$R_C = 25k - 15k$$

$$R_C = 10k\Omega$$

$$(I_E = (1 + \beta) I_B)$$

$$\text{From stage 2: } R_{in2} = R_S \parallel R_G \parallel \frac{\beta}{g_m} + (\beta + 1) R_E$$

$$= 91k \parallel 200k \parallel \frac{153.8}{0.385} + (154.8)(1k)$$

$$= 44.57k\Omega$$

$$\frac{1}{R_C} = \frac{1}{R_{C2}} + \frac{1}{R_{in3}}$$

$$R_{C2} \approx 13k\Omega$$

### $R_E$ for Stage 1 & 2

$$A_{v02} = \frac{V_3}{V_2} = \frac{-g_{m2}(R_{C2} \parallel R_{in3})}{1 + g_{m2} R_E}$$

$$-7.1 = \frac{-0.0154(13k \parallel 44.57k)}{1 + (0.0154) R_E}$$

$$R_E \approx 1353\Omega$$

$$R_{inL3} = 91k \parallel 200k \parallel \frac{153.8}{0.385} + (154.8)(500)$$

$$= 34.67k\Omega$$

$$A_{v2} = \frac{-0.0154(13k \parallel 34.67k\Omega)}{1 + 0.0154(1353)}$$

$$A_{v2} = -6.7$$

### RE for Stage 2

$$R_E = 1353 \Omega \approx 1.3 k\Omega$$

$$1.3 k = \frac{1}{\frac{1}{R_{B3}} + \frac{1}{R_{E4}}}$$

$$\frac{1}{1.3 k} = \frac{1}{15 k} + \frac{1}{R_{E4}}$$


$$R_{E4} \approx 1.3 k\Omega \quad (\text{rounded down since lower } R_E \text{ results to more gain})$$

### Biasing Resistors

Divider current  $\gg I_B$

Assume  $R_B = 91 k\Omega$

KVL @  $V_B$

 

$$\frac{4.25 - 10}{91 k} + \frac{4.25}{R_4} + 2 \mu A = 0$$


$$R_4 \approx 93 k\Omega$$

$$R_{in2} = R_3 \parallel R_4 \parallel \frac{\beta}{g_m} + (\beta + 1) R_E$$

$$= 91 k \parallel 93 k \parallel \frac{114.3}{0.0154} + (115.3)(1353)$$

$$\approx 31.433 k\Omega$$

KVL for Stage 1

 

$$-4.25 + 0.7 + I_E \cdot R_{E1} = 0$$

$$(1 + \beta) I_B R_{E1} = 5.55$$

$$(11.43 + 1)(2 \mu) R_{E1} = 5.55$$

$$R_{E1} \approx 15 k\Omega$$

$$I_{C,DC} = \frac{V_{CC}}{R_{E1} + R_C}$$

$$R_C + R_{E1} = \frac{10V}{100 \mu A} = 25 k\Omega$$

$$R_C = 25 k - 15 k$$

$$R_C = 10 k\Omega$$

$$R_C = R_{C1} \parallel R_{in2}$$

$$10 k = \frac{1}{\frac{1}{R_{C1}} + \frac{1}{31.433}}$$

$$R_{C1} \approx 15 k\Omega$$

$$A_{V1} = \frac{-g_m (R_{C1} \parallel R_{in2})}{1 + g_m R_E}$$

$$-7.1 = \frac{-0.0154 (14 k \parallel 31.433 k)}{1 + 0.0154 R_E}$$

$$R_E \approx 1.3 k\Omega$$

$$R_E = R_{E1} \parallel R_{E2}$$

$$\frac{1}{1.3 k} = \frac{1}{R_{E2}} + \frac{1}{15 k}$$

$$R_{E2} \approx 1.5 k\Omega$$

KCL @  $V_2$



$$\frac{4.25 - 10}{91k} + \frac{4.25}{R_2} + 2\mu A = 0$$

$$R_2 \approx 68k\Omega$$

$$R_{in} = 91k \parallel 68k \parallel \frac{\beta}{g_m} + (\beta+1)R_E$$

$$= 91k \parallel 68k \parallel \frac{100}{0.0054} + (101)(1299)$$

$$\approx 31.193k\Omega$$

## Capacitors

- $C_2, C_4, C_6$  must be large to maintain gain. ( $100\mu F$ )
- $C_1, C_3, C_5$  can be lower since  $R_{in1}, R_{in2}, R_{in3}$  are already high. ( $10\mu F$ )
- frequency:  $20Hz - 50kHz$
- $Z = \frac{1}{j\omega C}$

worst case:  $f = 20Hz$

$C_{2,4,6}$ :

$$Z = \frac{1}{j2\pi f C}$$

$$= \frac{1}{j2\pi (20)(100\mu F)}$$

$$= 79.6\Omega$$

$C_{1,3,5}$ :

$$Z = \frac{1}{j2\pi (20)(10\mu F)}$$

$$= 796\Omega$$

Best case:  $f = 50kHz$

$C_{2,4,6}$ :

$$Z = \frac{1}{j2\pi f C}$$

$$= \frac{1}{j2\pi (50)(100\mu F)}$$

$$= 31.8m\Omega$$

$C_{1,3,5}$ :

$$Z = \frac{1}{j2\pi (50)(10\mu F)}$$

$$= 0.32\Omega$$

From Calculated impedances, the selected capacitors  $10\mu F$  &  $100\mu F$  should maintain gain.

Final Gain:

$$A_{V0} = -7.1 \times -7.1 \times 1 = 50.41 \quad \text{within } 10\% \text{ of } 50$$

$$A_V = -6.7 \times -7.1 \times 1 = 47.57 \quad \text{within } 90\% \text{ of } A_{V0}$$

Quiescent current:

$$I_{DC, total} = I_{C1} + I_{R1} + I_{C2} + I_{R3} + I_{C3} + I_{R5}$$

$$= \beta I_{B1} + \frac{V_{CC}}{R_1 + R_2} + \beta I_{B2} + \frac{V_{CC}}{R_3 + R_4} + \beta I_{B3} + \frac{V_{CC}}{R_5 + R_6}$$

$$= 523mA < 10mA$$